

ELECENG 2EI4: Electronic Devices and Circuits 1

Design Project 2

Gurleen Kaur Rahi

Macid: rahig

400377038

Table of Contents

Test Plans.....	2
Switch Type1.....	3-5
Switch Type 2.....	6-9
AD2 Observations.....	10-13

Test Plan

Test Plan for Switch 1

For the closed switch state, V_{control} will be 0 v, and V_{supply} and V_1 will be equal to positive DC voltages. I will then measure the voltage across the p-mosfet and confirm that it is 0v, and $V_1 = V_2$.

In my test for the open switch state, I will set the V_{control} to 5V, and V_{supply} will again be a positive DC voltage equal to V_1 . Then, I will measure the current I_1 at V_1 and I_2 at V_2 , and make sure that they are almost equal to 0. I will achieve this by adding a load resistor at both V_1 and V_2 , and measuring the voltage drop across them. Using Ohm's law, I will calculate the current flowing through the resistors.

Test Plan for Switch 2

During my test to identify the closed switch state, I will set V_{control} to 0V, and V_{supply} to a positive DC voltage equivalent to V_1 . Then, I will use AD2 to measure the voltage at V_A and check whether it closely matches V_1 . Similarly, when determining the open switch state, I will set V_{control} to 5V, and V_{supply} to a positive DC voltage equivalent to V_1 . After that, I will utilize AD2 to measure the current at V_1 and V_B and ensure that both readings are nearly identical.

Switch Type 1

1. A circuit schematic of your design.

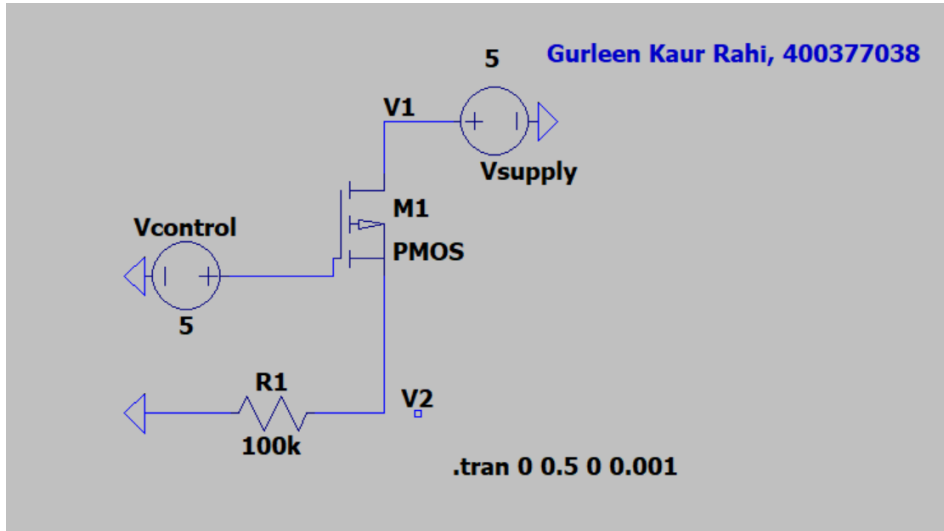


Figure 1: Switch 1 in the ON state

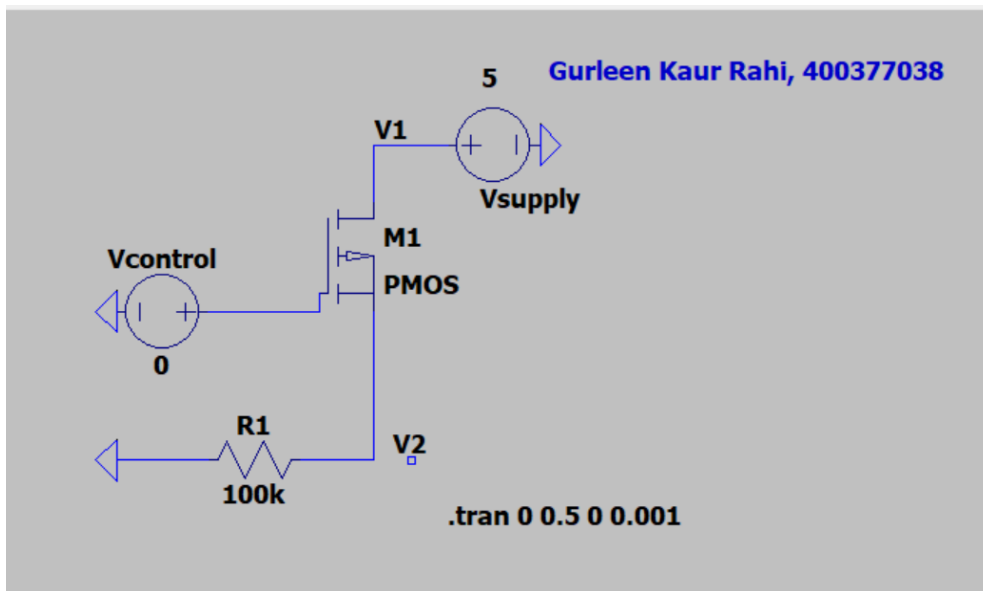


Figure 2: Switch 1 in the OFF state

2. Measurements performed according to the test plan.

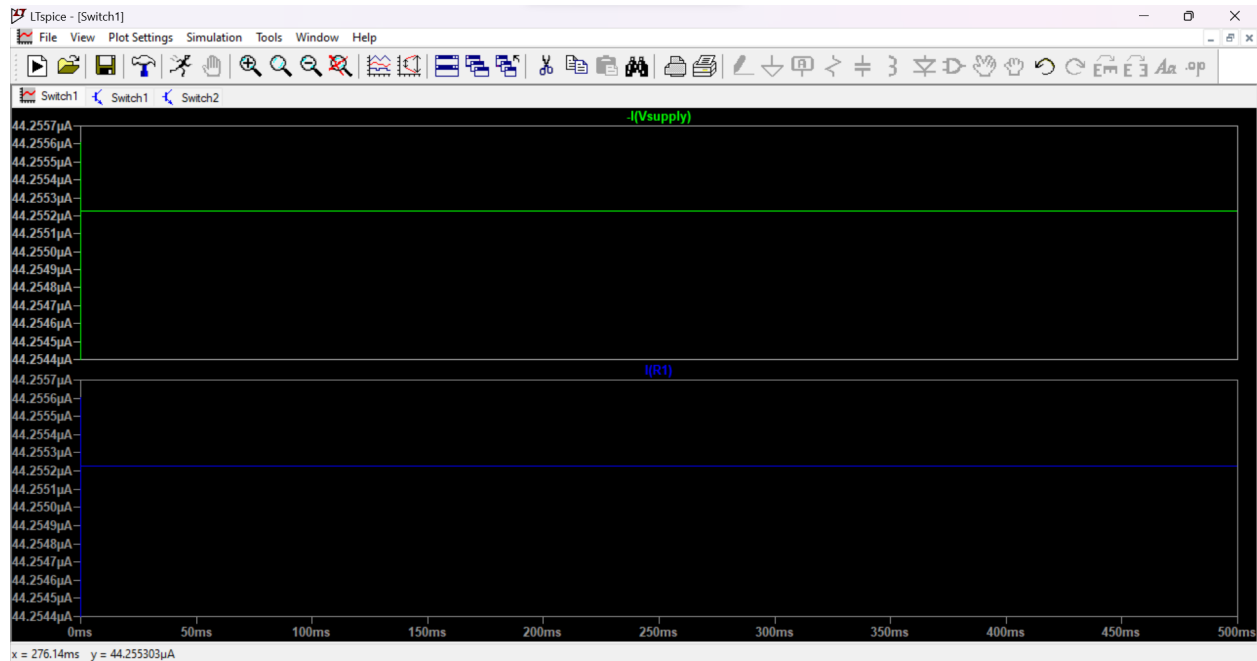


Figure 3: Graph simulation for Switch 1 in the ON state

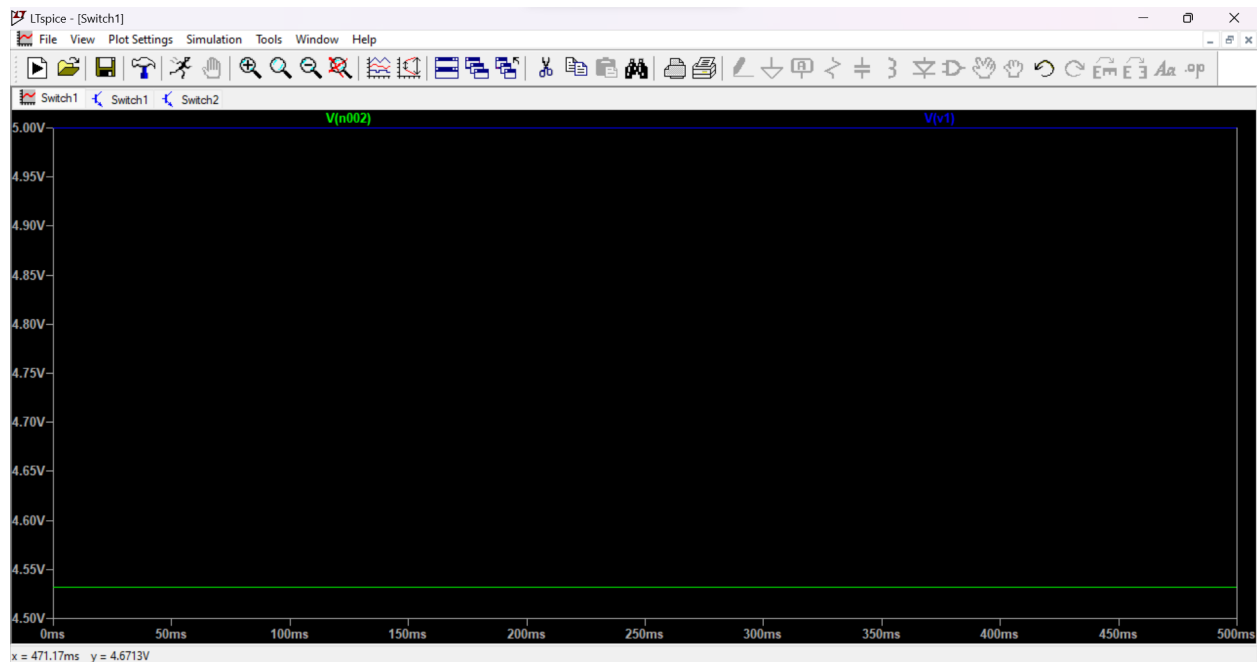


Figure 4: Graph simulation for Switch 1 in the OFF state

3. Theoretical explanation for the results obtained and comparison of the quantitative results with the theory.

When the switch is turned on, V_1 and V_2 are nearly equal in theoretical calculations. However, when measured using the AD2, V_2 is slightly lower at 4.3V when V_1 is 5V,

which is attributed to the internal resistance of the MOSFET. Conversely, when the switch is turned off, the measured values for I_1 and I_2 are both 0.05 mA instead of being precisely zero as expected in theory. This is because there is no current path when the switch is open. The measured values are close to zero, but there may be some minor inaccuracies caused by extra resistance in the circuit components.

4. Design tradeoffs. What tradeoffs did you make in your design for performance, complexity, and cost?

In my design, to increase the performance, I used a resistor of relatively higher resistance that will help the switch gain the properties of an ideal switch. To reduce complexity, I used only 1 MOSFET in my design so that there is a minimal amount of time delay (if any). Using only 1 MOSFET could be reasonable in terms of cost, however, using a resistor of higher value could be expensive.

Switch Type 2

1. A circuit schematic of your design.

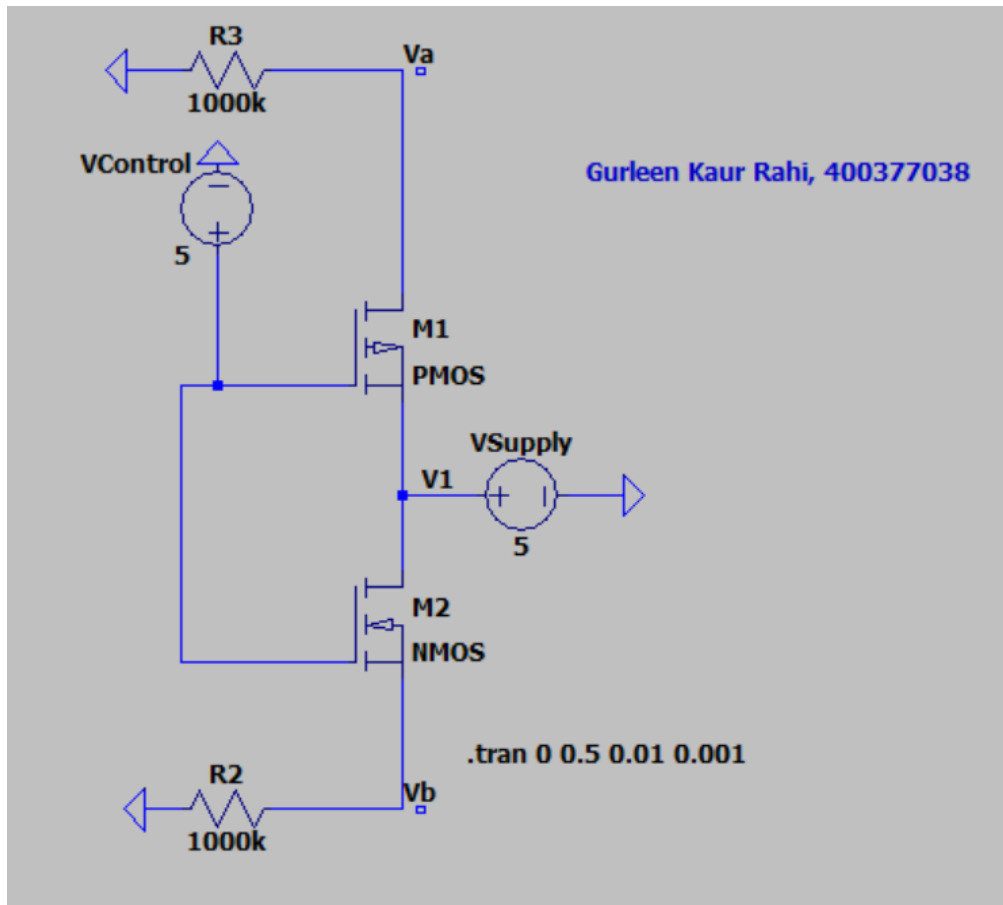


Figure 5: Switch 2 in the ON state

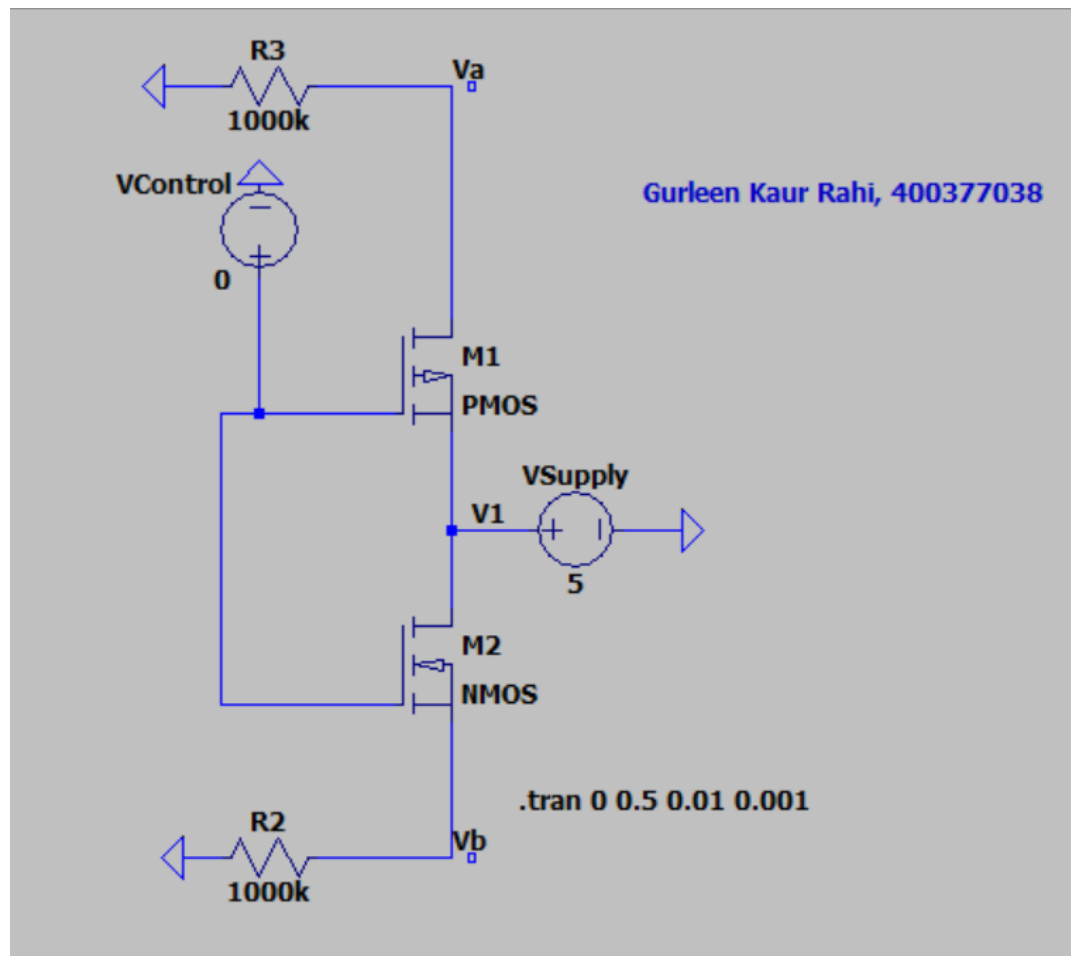


Figure 6: Switch 2 in the OFF state

2. Measurements performed according to the test plan.

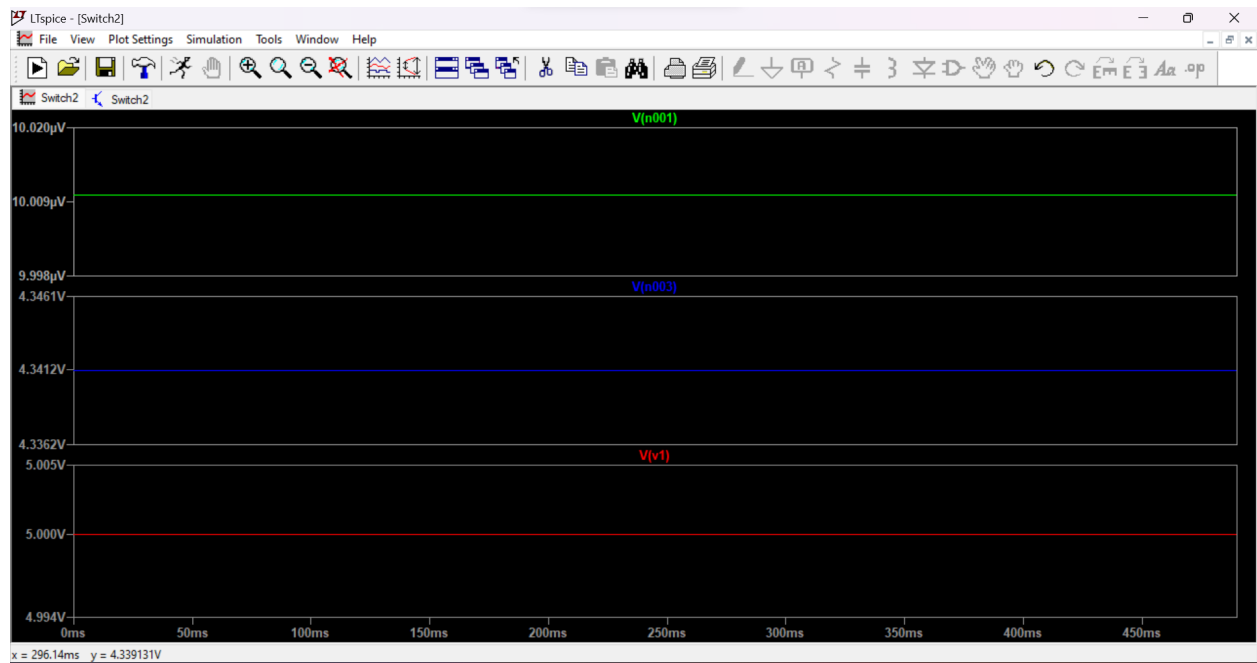


Figure 7: Graphical simulation for Switch 2 in ON state



Figure 7: Graphical simulation for Switch 2 in OFF state

3. Theoretical explanation for the results obtained and comparison of the quantitative results with the theory.

When V_{control} is at 0V, the switch links to the output V_A , and V_{supply} and V_A have values of 5V and 4.34V, respectively. In theory, V_{supply} and V_A should be identical since they belong to the same node. However, due to the internal resistance present in the MOSFET and wiring, they have a slight difference. The voltage values on either side of a closed switch should be equal. When V_{control} is at 5V, the switch links to output V_B , and both V_{supply} and V_B have values of 5V and 4.34V, respectively. V_{supply} and V_B should be the same as they are part of the same node. Nonetheless, there is still a small variation in their values due to the internal errors and resistances in the circuit components.

4. Design tradeoffs. What tradeoffs did you make in your design for performance, complexity, and cost?

The tradeoffs for this circuit design are quite similar to the previous circuit. The only difference is that in this design, I used two MOSFETS instead of one. I also removed one of the resistors because this will give me more accuracy as the value of V_a is 4.95 V which is very close to 5V. This will not only increase the cost of the design but also increase the complexity of the circuit. The circuit design seems to work very well with some minor simulation errors which might give rise to some uncertainties in the voltage values.

AD2 Observations

Switch 1

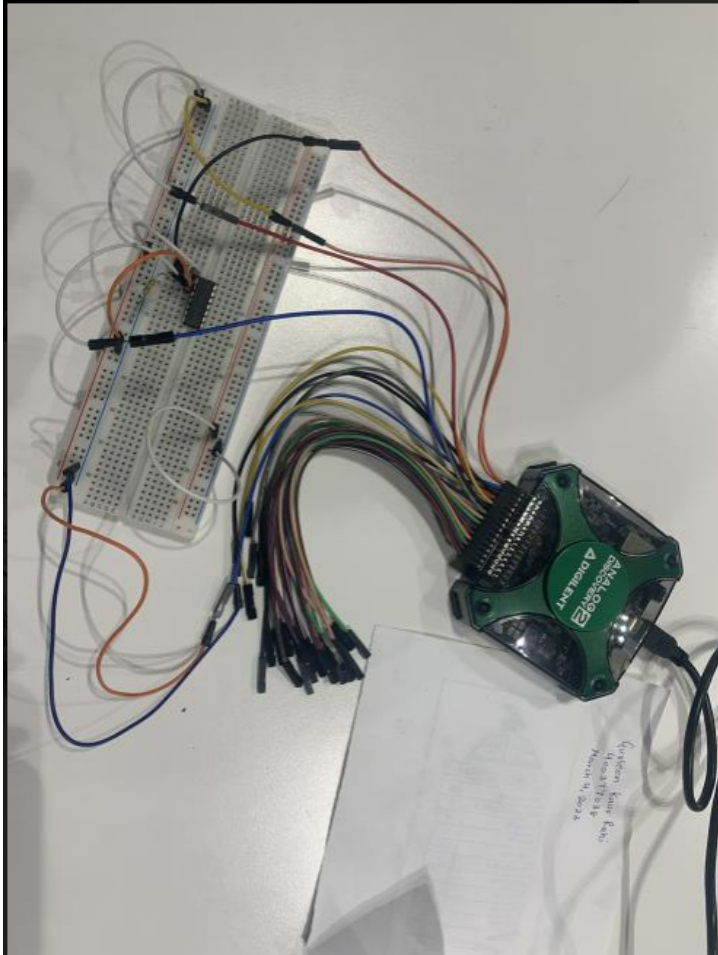


Figure 8: Physical circuit for Switch 1

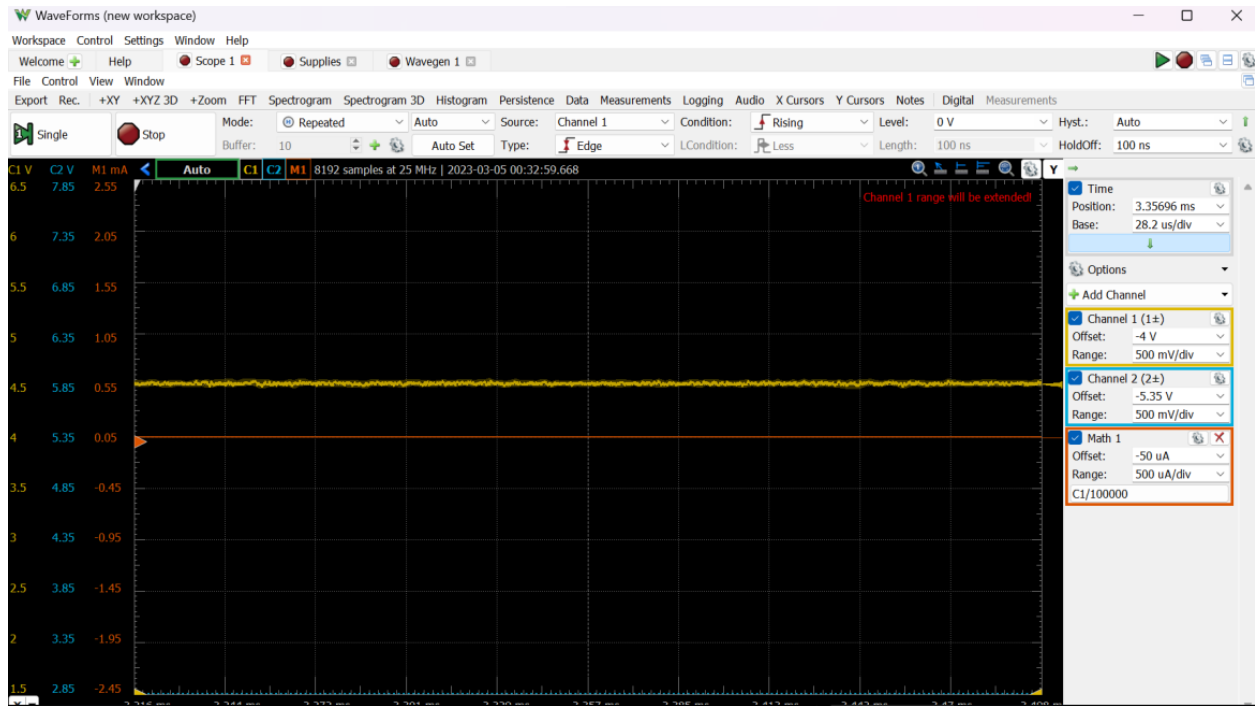


Figure 9: AD2 Waveform for Switch 1

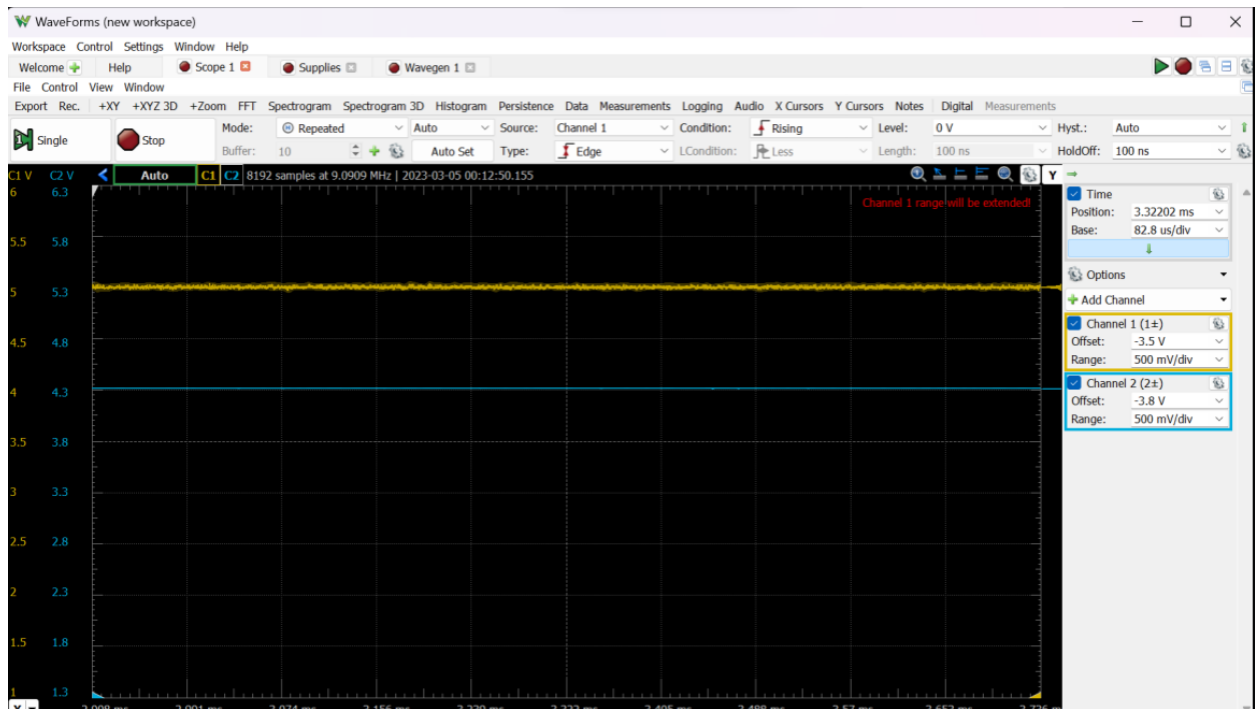


Figure 10: AD2 Waveform for Switch 1

Switch 2

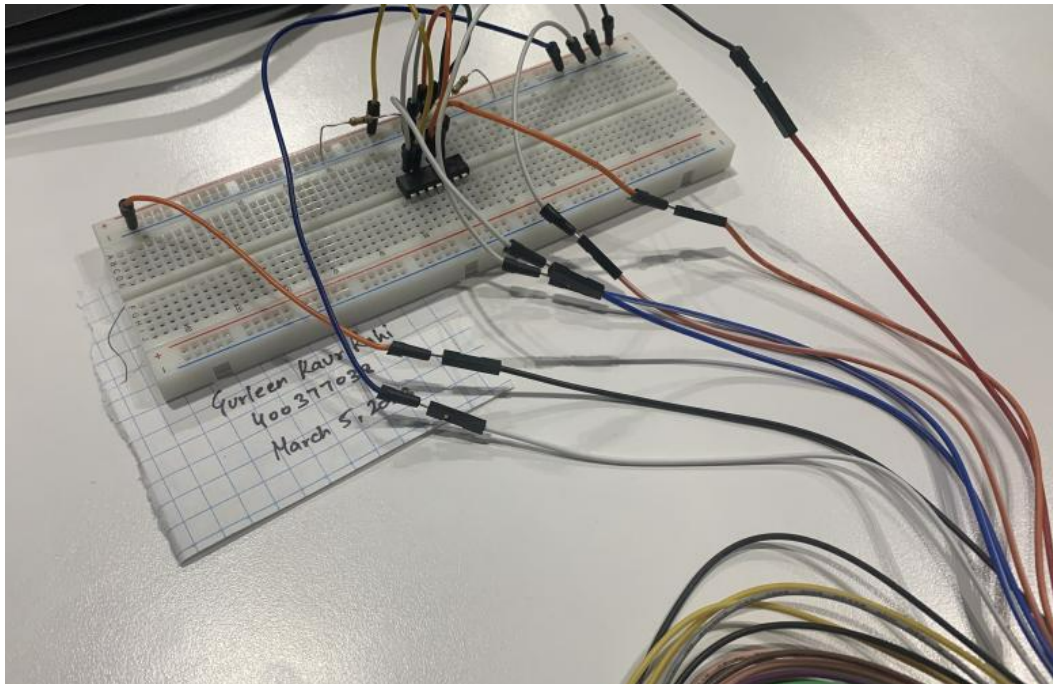


Figure 11: Physical circuit for Switch 2

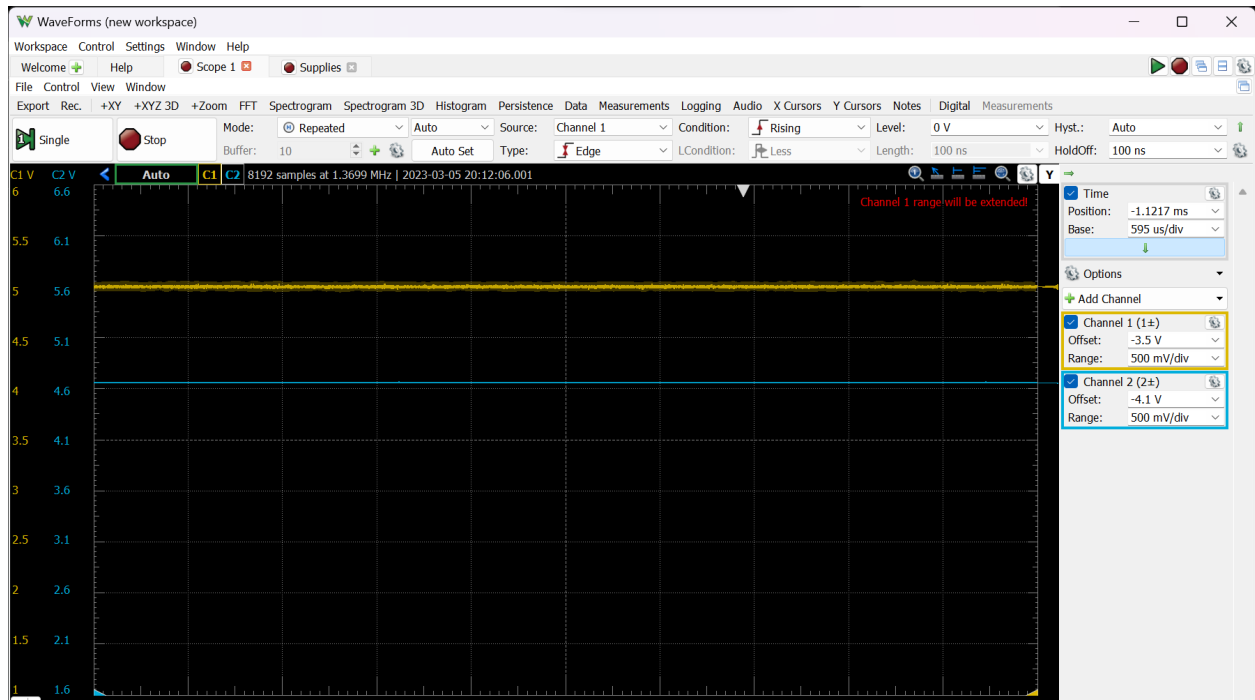


Figure 12: AD2 Waveform for Switch 2

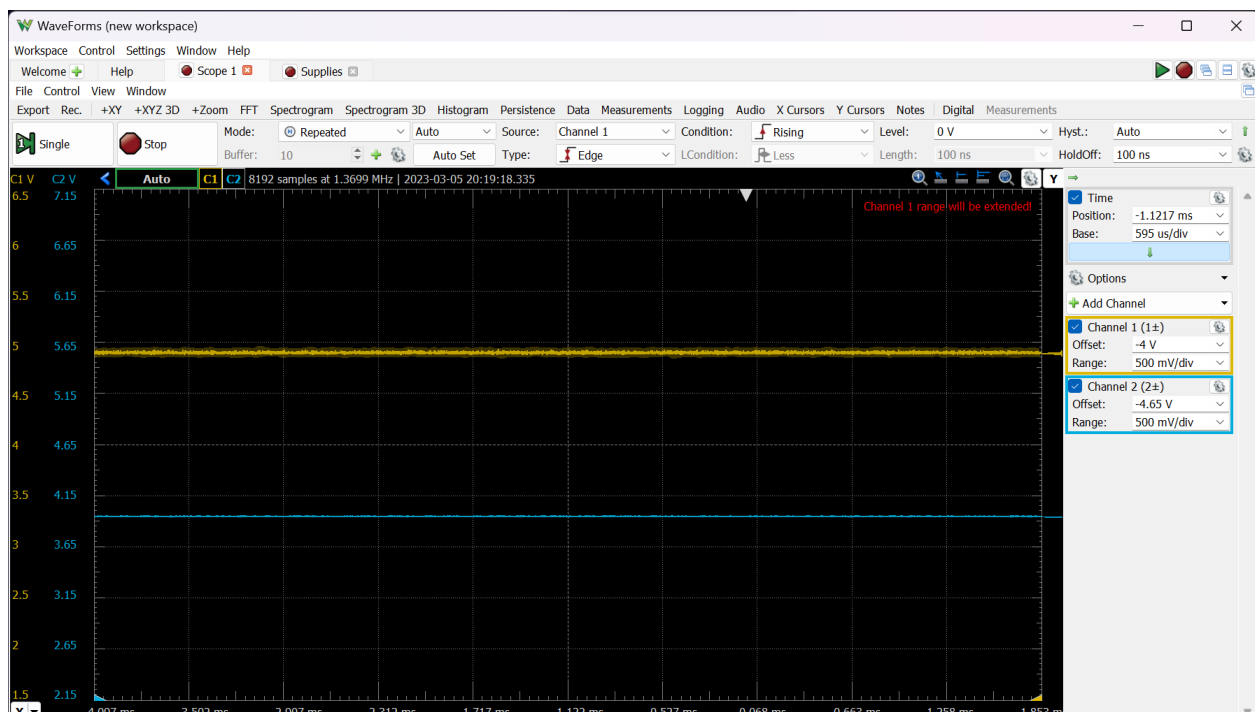


Figure 13: AD2 Waveform for Switch 2